

Duration: 3hrs

Max. Marks:80

NB:

- (1) Question No.1 is compulsory.
- (2) Answer any **three** from remaining questions.
- (3) **Figures** to the right indicate full marks.
- (4) Assume suitable data if required.

Q.1 Attempt any four

- a Compare JFET and MOSFET 5
- b Explain the Significance of stability factor 5
- c Why crystal oscillator is most stable oscillator? 5
- d Describe thermal runaway in BJT 5
- e What is clipping and clamping explain with one example. 5

Q.2

- a Draw BJT CE amplifier with any biasing circuit and derive expression for voltage gain, input impedance and output impedance. 10
- b What is Varactor diode? Explain construction and operation of varactor diode. 10

Q.3

- a Sketch the circuit of Wein Bridge Oscillator using BJT and derive an expression for the frequency of oscillation. 10
- b For Common source amplifier with N-channel EOMOSFET determine A_v , Z_i , and Z_o . 10
 $V_{DD}=21V, R_1=42K, R_2=33K, R_D=5K, R_S=1.5K$. The MOSFET parameters are:
 $V_{TN}=1.5V, K_n=0.5mA/V^2$

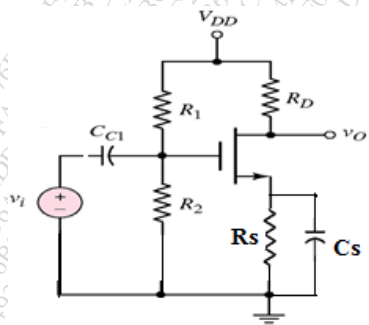


Fig.2

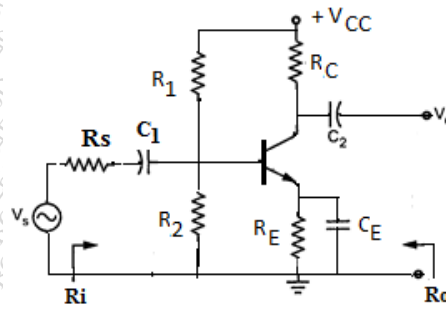


Fig.3

- Q.4** For the amplifier shown in Fig.3 analyze and determine. Derive the expression for small- 10
- a signal voltage gain, input and output impedance. BJT and circuit parameters are:
 $\beta = 100, V_{BE} = 0.7V, V_A = 100V, R_1=93.7K, R_2=6.3k, R_C=6K, R_S=0.5K, V_{CC}=12V$.
 - b Draw the constructional diagram of N-Channel JFET, and explain the operation and thus obtain the V-I characteristics. 10

Q.5

- a An N-Channel FET with common drain amplifier shown in fig.4 has the following parameters: $I_{DSS}=10\text{mA}$, at $V_P=-4\text{V}$. Determine Small signal voltage gain, input impedance and output impedance. If $R_1=10\text{M}$, $R_2=2\text{M}$, $V_{DD}=18\text{V}$, $R_S=1.2\text{k}$, $R_L=10\text{K}$. 10

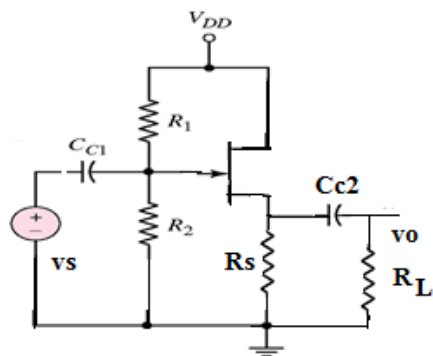


Fig.4

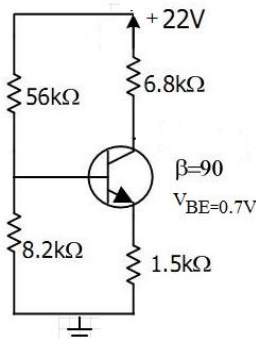


Fig.5

- b For the circuit shown in figure 5. Determine Q point co-ordinates. 10

Q.6

Attempt the following

- a) LC oscillator and its application. 5
- b) Small signal h- parameter parameters of BJT 5
- c) Depletion MOSFET operation. 5
- d) Compare BJT and FET 5


[Time: Three Hours]

[Marks:80]


N.B.

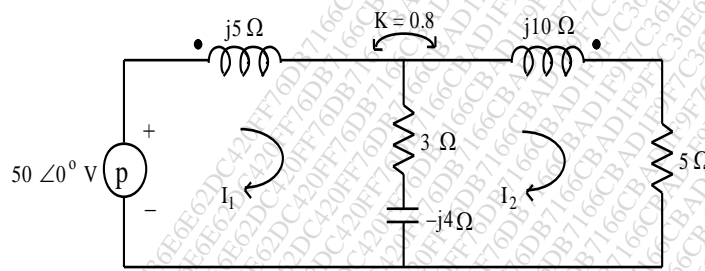- 1) Question No. 1 is Compulsory
- 2) Out of remaining questions, attempt any three
- 3) Assume suitable data if required
- 4) Figures to the right indicate full marks

1 (A) Draw equivalent circuit for given magnetically coupled circuit. 05




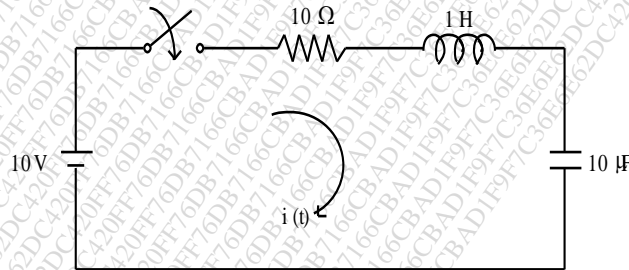(B) In the network shown in Fig., switch is closed. Assuming all initial conditions as zero, find i and $\frac{di}{dt}$ at $t = 0+$. 05




(C) In the two port network shown in Fig., compute h-parameters from the following data 05

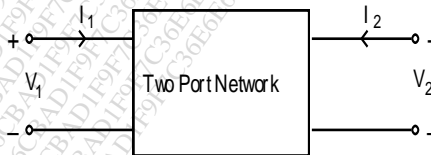- (a) With the output port short circuited : $V_1 = 25 \text{ V}$, $I_1 = 1 \text{ A}$, $I_2 = 2 \text{ A}$
- (b) With the input port open circuited : $V_1 = 10 \text{ V}$, $V_2 = 50 \text{ V}$, $I_2 = 2 \text{ A}$




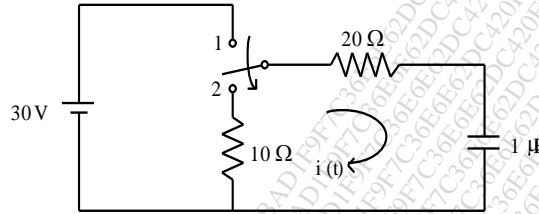(D) Design an m-derived T section high pass filter with a cut-off frequency of 2 kHz. Design impedance of 700Ω and $m = 0.6$. 05


- 2 (A) In the network shown in Fig., switch is changed from position 1 to position 2 at $t = 0$, steady condition having reached before switching. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0+$. 10



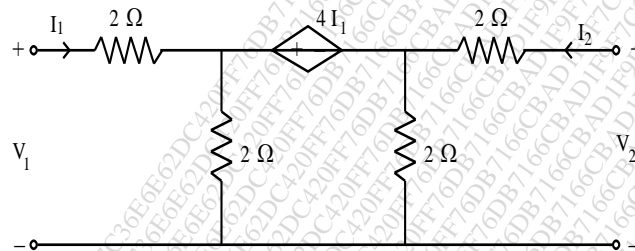- (B) Find Z and h-parameters for the network shown in Fig. 10



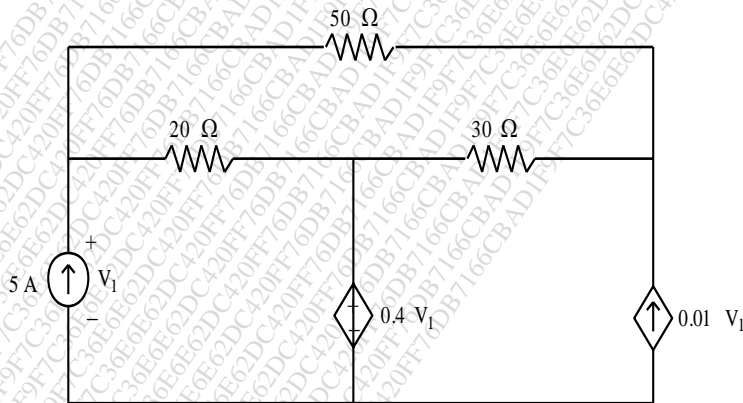- 3 (A) Find the power supplied by the dependent voltage source. 10




- (B) The parameters of a transmission lines are $R = 65\Omega/\text{km}$, $L = 1.6\text{mH}/\text{km}$, $G = 2.25\text{mmho}/\text{km}$, $C = 0.1\mu\text{F}/\text{km}$. Find 10

- i) Characteristic Impedance
- ii) Propagation Constant
- iii) Attenuation Constant
- iv) Phase Constant at 1 kHz


- 4 (A) Determine whether following functions are positive real 10

- i) $\frac{s^4 + 3s^3 + s^2 + s + 2}{s^3 + s^2 + s + 1}$
- ii) $\frac{s(s+3)(s+5)}{(s+1)(s+4)}$

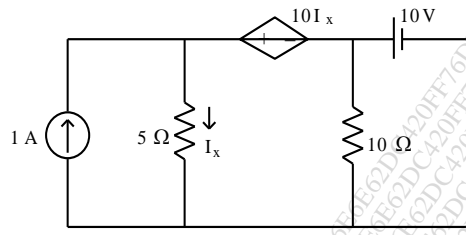(B) Obtain Thevenin equivalent network of Fig. 10



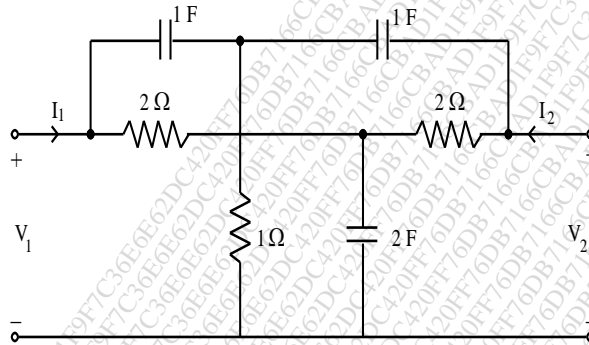5 (A) Find Y-parameters for the network shown in Fig. 10




(B) Realize the following functions in Foster II and Cauer I form 10

$$Z(s) = \frac{2(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

6 (A) A transmission line has a characteristics impedance of 50 ohm and terminate in a load $Z_L = 25 + j50$ ohm. Use smith chart and Find VSWR and Reflection coefficient at the load. 10

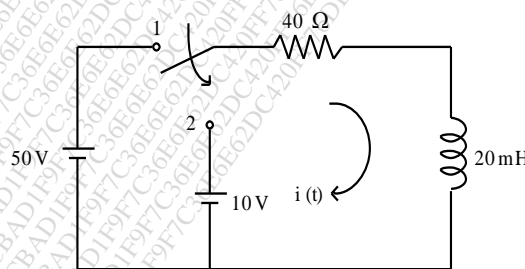(B) The network of Fig. is under steady state with switch at position 1. At $t = 0$, switch is moved to position 2. Find $i(t)$. 10



(3 Hours)

[Total Marks : 80]

Note:- 1) Question number 1 is compulsory.

2) Attempt any three questions from the remaining five questions

3) Figures to the right indicate full marks.

- Q.1 a) Find the Laplace transform of $\cos t \cos 2t \cos 3t$ 05
- b) Show that the set of functions $\cos nx$, $n = 1, 2, 3, \dots$ is orthogonal over $(0, 2\pi)$ 05
- c) Prove that $f(z) = (x^3 - 3xy^2 + 2xy) + i(3x^2y - x^2 + y^2 - y^3)$ is analytic and find $f'(z)$ in terms of z . 05
- d) Find the directional derivative of $\phi = x^2 + y^2 + z^2$ in the direction of the line $\frac{x}{3} = \frac{y}{4} = \frac{z}{5}$ at $(1, 2, 3)$ 05
- Q.2 a) Find the fourier series for $f(x) = x^2$ in $(0, 2\pi)$ 06
- b) Show that the vector $\vec{F} = (x^2 + xy^2) \mathbf{i} + (y^2 + x^2y) \mathbf{j}$ is irrotational and find its scalar potential 06
- c) Prove that the transformation $w = \frac{1}{z+i}$ transforms real axis of z - plane into a circle of w - plane 08
- Q.3 a) Using convolution theorem, find inverse Laplace transform of $\frac{s^2}{(s^2+2)^2}$. 06
- b) Prove that $J_{5/2}(x) = \sqrt{\frac{2}{\pi x}} \left(\frac{3-x^2}{x^2} \sin x - \frac{3}{x} \cos x \right)$ 06
- c) Find half range cosine series for $f(x) = x(\pi - x)$, $0 < x < \pi$. Hence show that $\sum_{n=1}^{\infty} \frac{1}{n^4} = \frac{\pi^4}{90}$ 08

Q.4 a) Evaluate by Green's theorem $\int_c (e^{x^2} - xy) dx - (y^2 - ax)dy$ where c is the circle $x^2 + y^2 = a^2$. 06

b) Prove that $2 J_0''(x) = J_2(x) - J_0(x)$. 06

c) i) Evaluate $\int_0^\infty \frac{e^{-t} - e^{-3t}}{t} dt$ 08

ii) Find Laplace transform of $t\sqrt{1 + \sin t}$

Q.5 a) Find the orthogonal trajectory of the family of curves $x^3y - xy^3 = c$. 06

b) Prove that $\int x \cdot J_{2/3}(x^{3/2}) dx = -\frac{2}{3} x^{-1/2} J_{-1/3}(x^{3/2})$. 06

c) Obtain complex form of Fourier Series for $f(x) = e^{2x}$ in $(0, 2)$. 08

Q.6 a) Use stoke's Theorem to evaluate $\int_C \vec{F} \cdot d\vec{r}$ where $\vec{F} = yz i + zx j + xy k$ 06

and C is the boundary of the circle $x^2 + y^2 + z^2 = 1$ and $z = 0$.

b) Find the fourier integral representation for 06

$$f(x) = e^{ax}, x \leq 0, a > 0$$

$$= e^{-ax}, x \geq 0, a > 0$$

Hence show that $\int_0^\infty \frac{\cos wx}{w^2 + a^2} dx = \frac{\pi}{2a} e^{-ax}, x > 0, a > 0$

c) Solve using Laplace transform $(D^2 + 2D + 5)y = e^{-t}\sin t$, where $y(0) = 0, y'(0) = 1$. 08
